

**K-316**

Total Page No. : 3]

[Roll No. ....]

**BCA-01**

**BCA Ist Semester  
Examination Dec., 2023**

**COMPUTER FUNDAMENTALS AND  
INTRODUCTION TO DIGITAL LOGIC**

**Time : 2 Hours]**

**[Max. Marks : 70**

---

*Note :- This paper is of Seventy (70) marks divided into two (02) Sections 'A' and 'B'. Attempt the questions contained in these Sections according to the detailed instructions given there in. Candidates should limit their answers to the questions on the given answer sheet. No additional (B) answer sheet will be issued.*

**Section-A**

**(Long Answer Type Questions) 2×19=38**

*Note :- Section 'A' contains Five (05) Long-answer type questions of Nineteen (19) marks each. Learners are required to answer any two (02) questions only.*

**K-316**

( 1 )

P.T.O.

1. Define Computer ? Also explain the various features of computer system.
2. Discuss various types of Logic Gates. Also discuss their applications.
3. Draw a block diagram of basic components of a computer system. Explain each component in detail.
4. Explain the block diagram of full adder,
5. What is flip-flop? Explain RS-flip flop and JK-flip-flop.

### **Section–B**

**(Short Answer Type Questions)**      4×8=32

**Note** :– Section ‘B’ contains Eight (08) Short-answer type questions of Eight (08) marks each. Learners are required to answer any *four* (04) questions only.

1. What is RAM & ROM ? Differentiate between both.
2. Explain about encoder and decoder.
3. Write down the difference between asynchronous and synchronous counter.
4. Explain about various generations of computers.
5. What is a RAM? What are its two types ? Differentiate between them.
6. Write a short note on Multiplexer and Demultiplexer.

7. What is sequential circuit ? How it differ from combinational circuit ?
8. Define the following terms :
  - (i) Address bus, Data bus, Control bus
  - (ii) Input and Output devices

\*\*\*\*\*