

Roll No.

BCA(N)-120

1st Semester Examination, 2023 (Dec.)

Digital Electronics

Time : 2 Hours]

[Max. Marks : 70

Note : This paper is of Seventy (70) marks divided into two (02) Sections A and B. Attempt the questions contained in these sections according to the detailed instructions given therein.

SECTION—A

(Long Answer Type Questions)

Note : Section 'A' contains Five (05) long answer type questions of nineteen (19) marks each. Learners are required to answer any two (02) questions only. $2 \times 19 = 38$

1. How will you convert R-S flip flop into J-K flip flop?
Also discuss characteristic table of J-K Flip flop.

BCA(N)-120/3

(1)

[P.T.O.]

2. A process is described by the logical expression : $Z = ABC + AC + AB'C$
Find the expression for the minimal sum of products using K-map and implement the result with the logic gates diagram.
3. Develop the truth table for the half-subtractor and write the logical expressions for the difference and borrow terms. Also suggest a circuit for this kind of function.
4. What is a ring counter? What type of flip-flop is used in such counters? Write one application of this counter.
5. Explain operation of a 4 bit left shift register. Also draw its timing diagram.

SECTION—B

(Short Answer Type Questions)

Note : Section 'B' contains Eight (08) short answer type questions of Eight (08) marks each. Learners are required to answer any Four (04) questions only.

$$4 \times 8 = 32$$

1. What is a binary code? Represent the decimal number 2934 in :
 - (a) BCD
 - (b) Excess-3 code

BCA(N)-120/3

(2)

2. Draw the logic diagram for the logic function
$$Z = (A + B + C).D$$
3. Differentiate between flip-flop & latches.
4. Explain the working of 4 * 1 multiplexer with the help of logic diagram and function table.
5. Differentiate between Asynchronous and Synchronous counter.
6. Perform the following subtraction : 100010 – 100110
 - (a) Using the 2's complement
 - (b) Using the 1's complements
7. What is a memory unit? Discuss the working of RAM and ROM using block diagram.
8. Minimize the following Boolean function using k map
$$F(A, B, C, D) = \Pi(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$$
