

A-0592

Total Pages : 3

Roll No.

MSCPH-509

M.Sc. PHYSICS (MSCPH)

(Electronics)

2nd Semester Examination, Session December 2024

Time : 2:00 Hrs.

Max. Marks : 70

Note :- This paper is of Seventy (70) marks divided into Two (02) Sections 'A' and 'B'. Attempt the questions contained in these Sections according to the detailed instructions given therein. Candidates should limit their answers to the questions on the given answer sheet. No additional (B) answer sheet will be issued.

Section-A

Long Answer Type Questions 2×19=38

Note :- Section 'A' contains Five (05) Long-answer type questions of Nineteen (19) marks each. Learners are required to answer any two (02) questions only.

1. Discuss construction, working and V-I characteristics of Zener diode ? Define voltage regulation. How zener diode used as a voltage regulator in power supply system.
2. Explain the input and output characteristics of a NPN transistor and discuss its working as an amplifier.
3. Discuss the construction and working of a field effect transistors ? Why they are named so ? Also discuss the drain characteristic of JFET and effect of pinch off voltage on its depletion region.
4. Describe the characteristics of an ideal Op-Amp and compare it with a practical Op-Amp IC741.
5. Explain the classification of Integrated Circuits (ICs) and discuss their construction techniques.

Section–B

Short Answer Type Questions 4×8=32

Note :- Section 'B' contains Eight (08) Short-answer type questions of Eight (08) marks each. Learners are required to answer any *four* (04) questions only.

1. What do you understand by Charged Coupled Devices (CCD).

2. What is the switching behavior of a transistor ? How is it applied in digital circuits ?
3. Define input resistance and output resistance in an amplifier. Why are these important ?
4. What are the different biasing schemes used in transistors ? Why is proper biasing necessary ?
5. What is feedback in an amplifier ? Explain the difference between positive and negative feedback.
6. What do you understand by zero crossing detector. Explain it.
7. What is the difference between single-ended and double-ended inputs in Op-Amps ?
8. Draw and label the pinout of IC741 and describe the function of any two pins.
