

**A-1136**

Total Pages : 4

Roll No. ....

**BCA (N)-120**

**Digital Electronics**

Examination February, 2026

Time : 2:00 Hrs.

Max. Marks : 70

*Note :-* This paper is of Seventy (70) marks divided into Two (02) Sections 'A' and 'B'. Attempt the questions contained in these Sections according to the detailed instructions given therein. *Candidates should limit their answers to the questions on the given answer sheet. No additional (B) answer sheet will be issued.*

**Section-A**

**(Long Answer Type Questions) (2×19=38)**

*Note :-* Section 'A' contains Five (05) Long-answer type questions of Nineteen (19) marks each. Learners are required to answer any *two* (02) questions only.

**A-1136**

( 1 )

P.T.O.

1. Explain all binary codes : BCD, Gray code, Excess-3 code, alphanumeric codes. Show conversions between binary  $\leftrightarrow$  BCD and binary  $\leftrightarrow$  Gray.
2. Define Boolean algebra. What is Huntington's postulates ? What are the several new proposition derived using the basic Huntington's postulates ?
3. Minimize the following Boolean function using 5-variable Karnaugh-map :  
$$F(A, B, C, D, E) = \Sigma m(1, 3, 4, 5, 7, 9, 12, 13, 16, 17, 19, 23, 25, 29).$$
4. What are combinational circuits ? Explain multiplexer, demultiplexer, encoder, and decoder with diagrams and applications.
5. Explain in detail the working of MOD-10 counter, ring counter, and Johnson counter with diagrams.

### Section–B

(Short Answer Type Questions) (4×8=32)

**Note** :- Section 'B' contains Eight (08) Short-answer type questions of Eight (08) marks each. Learners are required to answer any *four* (04) questions only.

1. Explain the steps of the Quine-McClusky method of minimization.
2. Write short notes on the following :
  - (a) Logic gates
  - (b) Truth tables
3. What is flash memory ? Explain its features.
4. Explain half adder and full adder with truth tables.
5. Distinguish between SRAM and DRAM.
6. Write a short note on incompletely specified Boolean functions.
7. Explain master- slave JK flip-flop.
8. What is memory expansion ? Explain with an example.

\*\*\*\*\*

