

**A-1181**

Total Pages : 3

Roll No. ....

**MSCPH-509**

**M.Sc. Physics (MSCPH)**

**Electronics**

Examination February, 2026

Time : 2:00 Hrs.

Max. Marks : 70

*Note :-* This paper is of Seventy (70) marks divided into Two (02) Sections 'A' and 'B'. Attempt the questions contained in these Sections according to the detailed instructions given therein. *Candidates should limit their answers to the questions on the given answer sheet. No additional (B) answer sheet will be issued.*

**Section-A**

**(Long Answer Type Questions) (2×19=38)**

*Note :-* Section 'A' contains Five (05) Long-answer type questions of Nineteen (19) marks each. Learners are required to answer any *two* (02) questions only.

**A-1181**

( 1 )

P.T.O.

1. Describe the construction and working of a Zener diode. Draw its V-I characteristics and explain. Discuss Zener diode as a voltage regulator.
2. What is a transistor biasing ? What are the main reasons behind using the biasing circuits ? Discuss the voltage divider bias of transistor. Derive the expressions for stability factor and collector current.
3. Describe the following :
  - (i) Characteristics of FET
  - (ii) Applications of FET
  - (iii) Parameters of FET
  - (iv) Advantages and disadvantages of FET
4. What is operational amplifier ? Discuss ideal characteristics of an Op-amp and the implications of these characteristics on circuit analysis with neat diagram.
5. What is an integrated circuit ? Give their classification and discuss the making of monolithic IC.

### **Section–B**

**(Short Answer Type Questions) (4×8=32)**

**Note** :- Section ‘B’ contains Eight (08) Short-answer type questions of Eight (08) marks each. Learners are required to answer any *four* (04) questions only.

1. Explain the principle of photodiode.
2. What is distortion ? Explain the concept of harmonic distortion.
3. Give the advantages and applications of MOSFET.
4. Give the comparison of N-channel with P-channel FETs.
5. Explain the concept of an ideal op-amp and list the assumptions made when analyzing it.
6. Explain the role of “virtual short” concept in analyzing inverting and non-inverting op-amp configuration. How does this concept simplify the derivation of gain formulae ?
7. What is an IC ? Give advantages of ICs.
8. What are charge couple devices ? Explain.

\*\*\*\*\*